

--	--	--	--	--	--	--	--

G. VENKATASWAMY NAIDU COLLEGE (AUTONOMOUS), KOVILPATTI – 628 502.



UG DEGREE END SEMESTER EXAMINATIONS - NOVEMBER 2024.

(For those admitted in June 2021 and later)

PROGRAMME AND BRANCH: B.Sc., PHYSICS

SEM	CATEGORY	COMPONENT	COURSE CODE	COURSE TITLE
V	PART - III	CORE	U21PH508	FUNDAMENTALS OF ELECTRONICS

Date & Session: 05.11.2024/FN

Time: 3 hours

Maximum: 75 Marks

Course Outcome	Bloom's K-level	Q. No.	SECTION - A (10 X 1 = 10 Marks) Answer <u>ALL</u> Questions.
CO1	K1	1.	Give an example for current source. a) alternator b) generator c) battery d) photovoltaic cell
CO1	K2	2.	_____ represents the relationship between voltage and current in a two-port network. a) o-parameter b) n-parameter c) h-parameter d) m-parameter
CO2	K1	3.	A crystal diode is used as a/an _____. a) oscillator b) amplifier c) filter d) rectifier
CO2	K2	4.	A _____ allows ac and blocks dc. a) capacitor b) inductor c) transistor d) transformer
CO3	K1	5.	The built-in potential of a silicon diode at room temperature is _____. a) 0.7 V b) 0.3 V c) 1 V d) 10 V
CO3	K2	6.	The electric power is given by, $P =$ _____. a) i/R b) i^2R c) R/i d) R^2i
CO4	K1	7.	The operation of a bistable multivibrator is identical to that of a _____. a) register b) flip-flop c) converter d) counter
CO4	K2	8.	RC phase shift oscillators contain a minimum of _____ phase shift network. a) three b) two c) one d) zero
CO5	K1	9.	The _____ amplifier amplifies the difference between two input signals. a) log b) antilog c) differential d) buffer
CO5	K2	10.	The maximum rate at which the output voltage can change within its linear region is known as _____ of the op-amp. a) closed loop gain b) open loop gain c) slew rate d) CMRR
Course Outcome	Bloom's K-level	Q. No.	SECTION - B (5 X 5 = 25 Marks) Answer <u>ALL</u> Questions choosing either (a) or (b)
CO1	K3	11a.	Explain the maximum power transfer theorem. (OR)
CO1	K3	11b.	Develop the procedure for finding Norton equivalent circuit.
CO2	K3	12a.	Describe an experiment to draw the VI characteristics of a zener diode. (OR)
CO2	K3	12b.	Find an expression for efficiency of a half wave rectifier.

CO3	K4	13a.	Analyze the action of transistor with neat circuit diagram. (OR)
CO3	K4	13b.	Examine the function of Class B power amplifier.
CO4	K4	14a.	Explain Barkhausen conditions for an oscillation. (OR)
CO4	K4	14b.	Assess the clipping circuits with necessary input and output waveforms.
CO5	K5	15a.	Infer the application of op-amp as an integrator with its input and output waveforms. (OR)
CO5	K5	15b.	Elaborate in detail about the high pass filter with neat diagram.

Course Outcome	Bloom's K-level	Q. No.	SECTION - C (5 X 8 = 40 Marks) Answer <u>ALL</u> Questions choosing either (a) or (b)
CO1	K3	16a.	Briefly explain the conversion of voltage source into current source. (OR)
CO1	K3	16b.	Illuminate Thevenin's theorem with an example.
CO2	K4	17a.	Derive an expression for the efficiency of a bridge rectifier with neat sketch. (OR)
CO2	K4	17b.	Infer the operation of capacitor and choke input filter.
CO3	K4	18a.	Analyze the characteristics of JFET in detail. (OR)
CO3	K4	18b.	Examine the function of RC coupled amplifier with neat diagram.
CO4	K5	19a.	Predict the function of Hartley oscillator and obtain its frequency. (OR)
CO4	K5	19b.	Assess the operation of an a stable multivibrator with neat diagram.
CO5	K5	20a.	Draw an op-amp circuit whose output is $V_0 = - (V_1+V_2+V_3)$. (OR)
CO5	K5	20b.	(a) Derive an expression for the voltage gain of non-inverting amplifier with neat diagram. (b) In a non-inverting amplifier, let $R_1 = 5k\Omega$, $R_f = 20k\Omega$ and $V_i = 1V$. A load resistor of $5k\Omega$ is connected at the output. Calculate the output voltage.